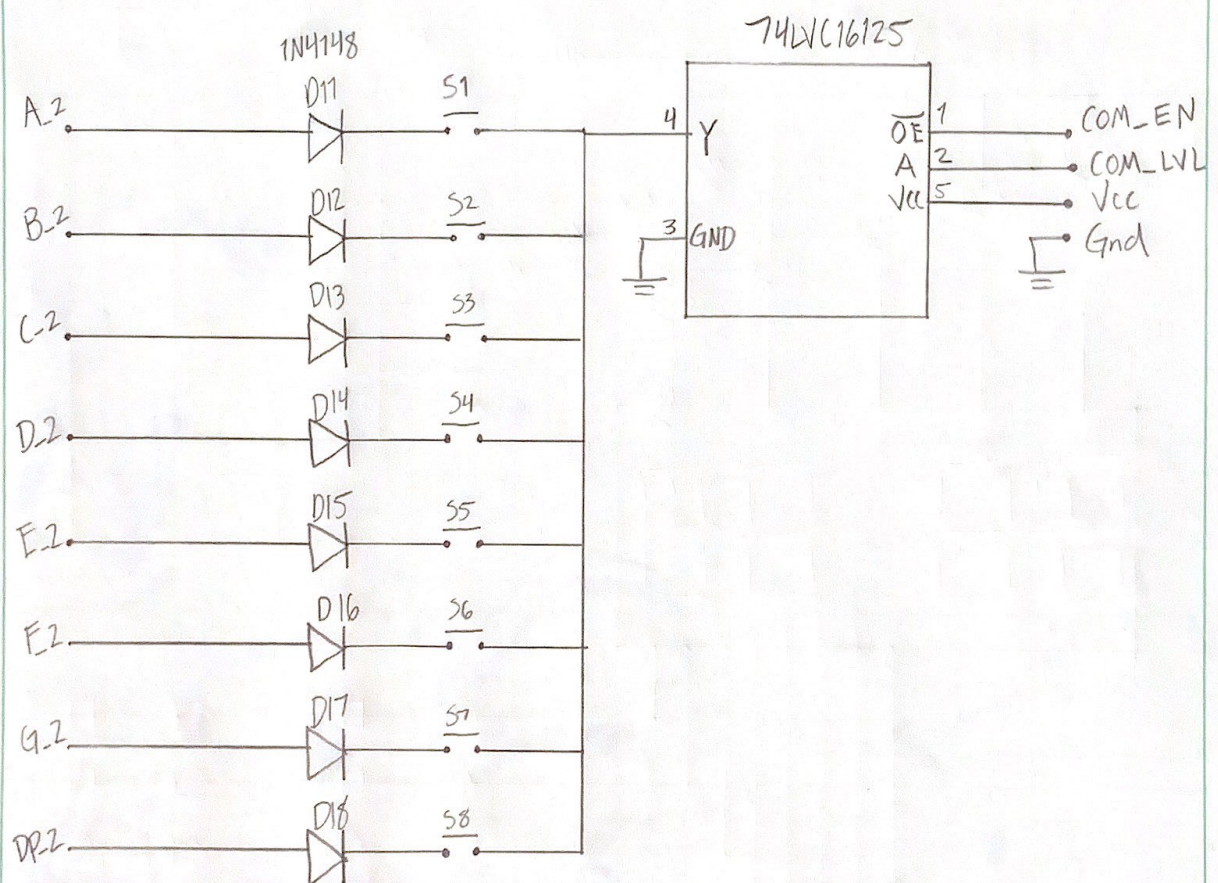



System diagram

# Button Board





## Display Board

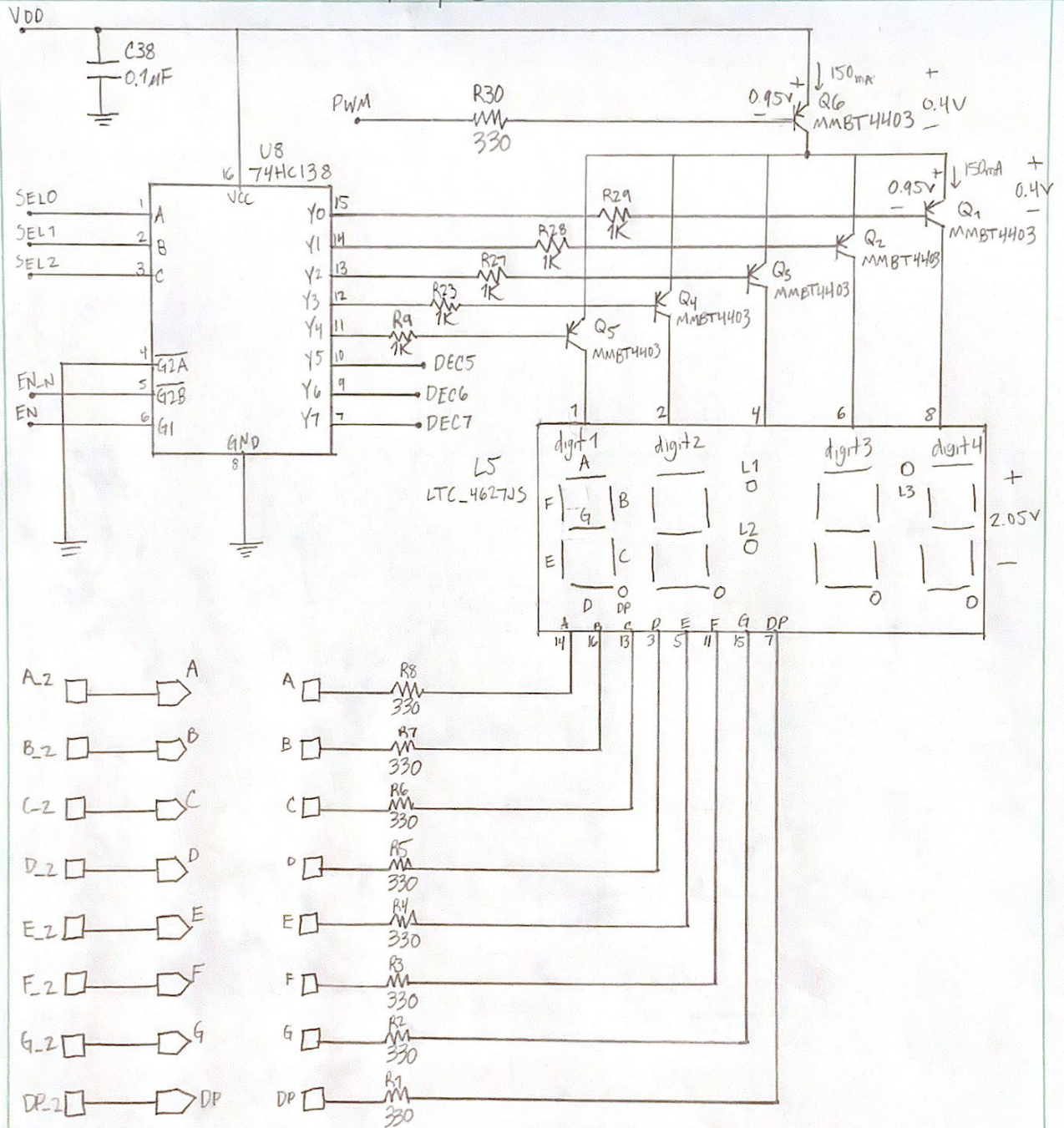



## Calculations

Max Current through PA0-PA7: 40 mA

Current through each segment: 20 mA @  $V_F = 2.05$  (typ.)

$$\therefore |I_{Q_6}| = 20 \text{ mA} (8)$$

$$= 160 \text{ mA}$$

need about 160 mA through  $Q_6$  to light up all segments

From data sheet:  $V_{CE_{sat}} = -0.4 \text{ V}$  @  $I_C = -150 \text{ mA}$ ,  $I_B = -15 \text{ mA}$

$$R_{1-8} = \frac{5 \text{ V} - 0.8 \text{ V} - 2.05 \text{ V}}{150 \text{ mA} / 8} \cong 115 \Omega$$

$$V_{BE_{sat}} = -0.95 \text{ V} @ I_C = -150 \text{ mA}, I_B = -15 \text{ mA}$$

$$R_{9-29} = \frac{5 \text{ V} - 0.4 \text{ V} - 0.95 \text{ V}}{15 \text{ mA}} \cong 243 \Omega$$

$$R_{30} = \frac{5 \text{ V} - 0.95 \text{ V}}{15 \text{ mA}} \cong 270 \Omega$$

Worst case analysis: One segment on

From data sheet:  $V_{CE_{sat}} \cong -0.05 \text{ V}$  @  $I_C = -20 \text{ mA}$

$$I_{R_{1-8}} = \frac{5 \text{ V} - 0.1 \text{ V} - 2.05 \text{ V}}{115 \Omega} \cong 24.78 \text{ mA} < 40 \text{ mA}$$

(Max current through  
Atmega I/O pins)

$$V_{BE_{sat}} \cong -0.75 \text{ V} @ I_C = -20 \text{ mA}$$

$$I_{R_{9-29}} = \frac{5 \text{ V} - 0.05 \text{ V} - 0.75 \text{ V}}{243 \Omega} \cong 17.25 \text{ mA} < 25 \text{ mA}$$

(Max current through  
74HC138 output pins)