





Calculations

$$P_{\text{speaker}} = 200 \text{ mW Rms}$$

$$V_{\text{RMS}}^2 R = P_{\text{speaker}}$$

$$V_{\text{RMS}} = \sqrt{P_{\text{speaker}} (R)}$$

$$V_{\text{pp}} = 2\sqrt{2} V_{\text{RMS}}$$

$$V_{\text{pp}} = 2\sqrt{2} \sqrt{P_{\text{speaker}} (R)}$$

$$\text{Gain}_{\text{dB}} = 20 \text{ dB (Datasheet)}$$

$$20 \log_{10} \left(\frac{V_{\text{pp}}}{V_{\text{pre}}} \right) = 20$$

$$\frac{V_{\text{pp}}}{V_{\text{pre}}} = 10$$

$$V_{\text{pre}} = \frac{V_{\text{pp}}}{10}$$

$$V_{\text{pre}} = \frac{2\sqrt{2} \sqrt{P_{\text{speaker}} (R)}}{10}$$

$$V_{\text{pre}} \approx 0.35778 V_{\text{pp}}$$

$$\left| \frac{V_{\text{pre}}}{V_{\text{in}}} \right| = \frac{R_f}{R_1}$$

$$\left| \frac{0.35778 V_{\text{pp}}}{5 V_{\text{pp}}} \right| = \frac{R_f}{R_1}$$

$$R_1 = \frac{5}{0.35778} R_f$$

$$\text{Choose } R_f = 220 \Omega$$

$$\Rightarrow R_1 = R_2 \approx 3075 \Omega$$

$$\text{Choose } R_1 = R_2 = 10 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega \approx 3.2 \text{ k}\Omega$$

$C_1 + R_1$ form a high pass filter:

$$f_c = \frac{1}{2\pi R_1 C_1}$$

$$C_1 = \frac{1}{2\pi f_c R_1}$$

We want to play a wide range of tones, so we want the lowest f_c possible.

$$C \propto \frac{1}{f_c}$$

\Rightarrow we want the biggest C possible.

Choose biggest value in kit:

$$C_1 = 47 \mu\text{F}$$

Calculations

$R_3 + C_2$ form another high pass filter

$$f_c = \frac{1}{2\pi R_3 C_2}$$

Choose $C_2 = 0.1 \mu\text{F}$, $R_3 = 1\text{k}\Omega$:

$$f_c = \frac{1}{2\pi (1\text{k}\Omega)(0.1 \mu\text{F})} \cong 1592 \text{ Hz}$$

Using a PWM frequency of 16 MHz and cutoff of 1592 Hz ensures good ripple for the volume.